

07 – Binary systems, electronics and microprocessors

If it is not true then, it is false...


Jérôme Landré – jerome.landre@ju.se

OUTLINE

- 1) Two-state systems
- 2) Boolean Algebra
- 3) Logic circuits
- 4) Microprocessors

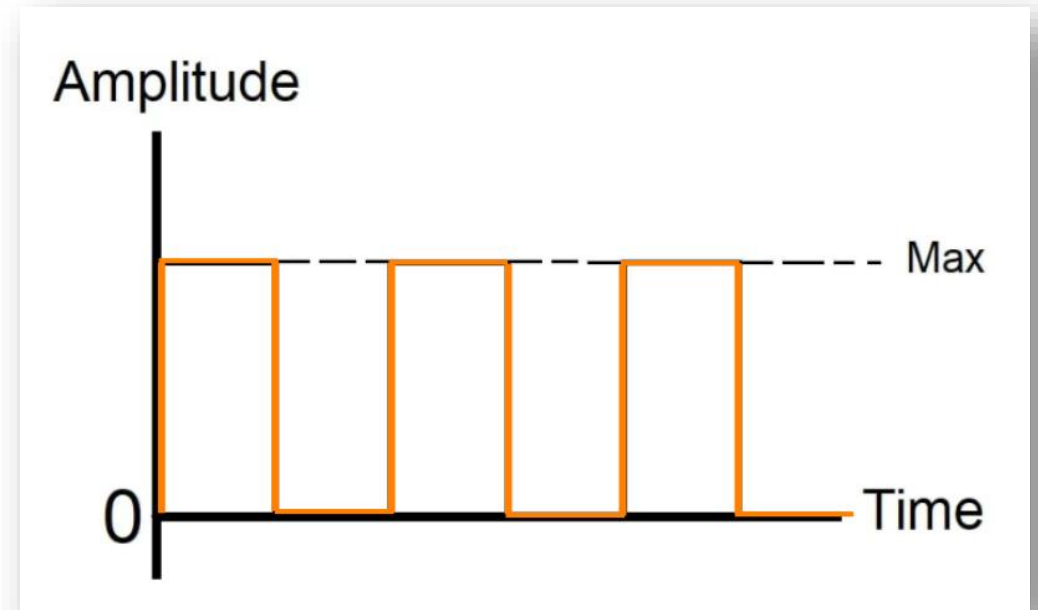1) TWO-STATE SYSTEMS

- The binary system works with two states: 0/1, false/true, off/on, open/closed, low/high
- An electric cable can have or not an electric current going through it
- When the Amplitude is maximum: 1
- When the Amplitude is minimum: 0



1) TWO-STATE SYSTEMS

- With one cable, you can represent ____ states: 0 or 1
- With two cables, you can represent ____ states:
- With three cables, you can represent ____ states:
- ...
- With N cables, you can represent ____ states:

1) TWO-STATE SYSTEMS

MSB

LSB

1 0 1 1 0 1 0 1 =

BINARY

DECIMAL

1) TWO-STATE SYSTEMS

- Introducing a new notation with the base as subscript:

$(1\ 1\ 0\ 0\ 1)_2$

BINARY

$(1\ 1\ 0\ 0\ 1)_{10}$

DECIMAL

1) TWO-STATE SYSTEMS

- Size of binary numbers:
 - 8 bits, 256 possible values (2^8)
 - 16 bits, 65 536 possible values (2^{16})
 - 32 bits, 4 294 967 396 possible values (2^{32})
 - 64 bits, 18 446 744 073 709 551 616 possible values (2^{64})

1) TWO-STATE SYSTEMS

- Names of binary numbers:
 - 1 binary digit: 1 bit (**b**inary digit)
 - 4 bits : a quad
 - 8 bits : a byte
 - 16 bits : a word
 - 32 bits : a double word
 - 64 bits : a quad word

1) TWO-STATE SYSTEMS

- How do you know if a binary number is odd or even? (at first glance)

Odd or Even?

- $(1\ 0\ 1\ 1)_2 =$
- $(10\ 1\ 0\ 1\ 1)_2 =$
- $(1\ 0\ 1\ 1\ 1\ 0)_2 =$
- $(1\ 0\ 1\ 0\ 1\ 1\ 0\ 1)_2 =$
- $(1\ 0\ 0\ 1\ 1\ 0\ 0\ 0\ 1\ 0\ 1\ 1)_2 =$
- $(1\ 0\ 1\ 0\ 1\ 1\ 0\ 0\ 0\ 1\ 0\ 0)_2 =$

1) TWO-STATE SYSTEMS

- What happen if you shift a binary number one position to the left?
- $(1\ 0\ 1\ 1)_2 =$
- $(1\ 0\ 1\ 1\ 0)_2 =$
- What happen if you shift a binary number one position to the right?
- $(1\ 0\ 1\ 0)_2 =$
- $(1\ 0\ 1)_2 =$
- What happen if you shift a binary number N positions to the left?
- What happen if you shift a binary number N positions to the right?

2) BOOLEAN ALGEBRA

- In 1854, George Boole defines boolean algebra to compute and to use functions with binary numbers
- It is based on three basic functions:
 - AND
 - OR
 - NOT

2) BOOLEAN ALGEBRA

- Truth tables:


Source: https://en.wikipedia.org/wiki/Boolean_algebra

a	$\overline{a}$ NOT a
0	1
1	0

a	b	$a.b$ a AND b
0	0	0
0	1	0
1	0	0
1	1	1

a	b	$a+b$ a OR b
0	0	0
0	1	1
1	0	1
1	1	1

Logic gates:

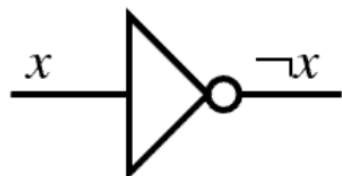

2) BOOLEAN ALGEBRA

- Laws:

	AND	OR
Identity	$1.a =$	$0+a =$
Annihilator	$0.a =$	$1+a =$
Idempotence	$a.a =$	$a+a =$
Complementation	$a.\bar{a} =$	$a+\bar{a} =$
Commutativity	$a.b =$	$a+b =$
Associativity	$a.(b.c) =$	$a+(b+c) =$
Absorption	$a.(a+b) =$	$a+(a.b) =$
Distributivity	$a.(b+c) =$	$a+(b.c) =$

2) BOOLEAN ALGEBRA

- Other laws:

$$\overline{\overline{a}} =$$

De Morgan laws:

$$\overline{a.b} =$$

$$\overline{a+b} =$$

Exclusive OR:

a	b	$a \oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

$$a \oplus b = (a + b).(\overline{a.b})$$

$$a \oplus b = \overline{(a.\bar{b}) + (\bar{a}.b)}$$

$$a \oplus b = ((a.b) + (\bar{a}.\bar{b}))$$

$$a \oplus b = (a + b).(\bar{a} + \bar{b})$$

2) BOOLEAN ALGEBRA

- Not OR (NOR):

a	b	$\overline{(a + b)}$
0	0	1
0	1	0
1	0	0
1	1	0


- Not AND (NAND):

a	b	$\overline{(a.b)}$
0	0	1
0	1	1
1	0	1
1	1	0

Theorem: **EVERY** logic function can be designed from **NOR** and **NAND** logical operators!

2) BOOLEAN ALGEBRA

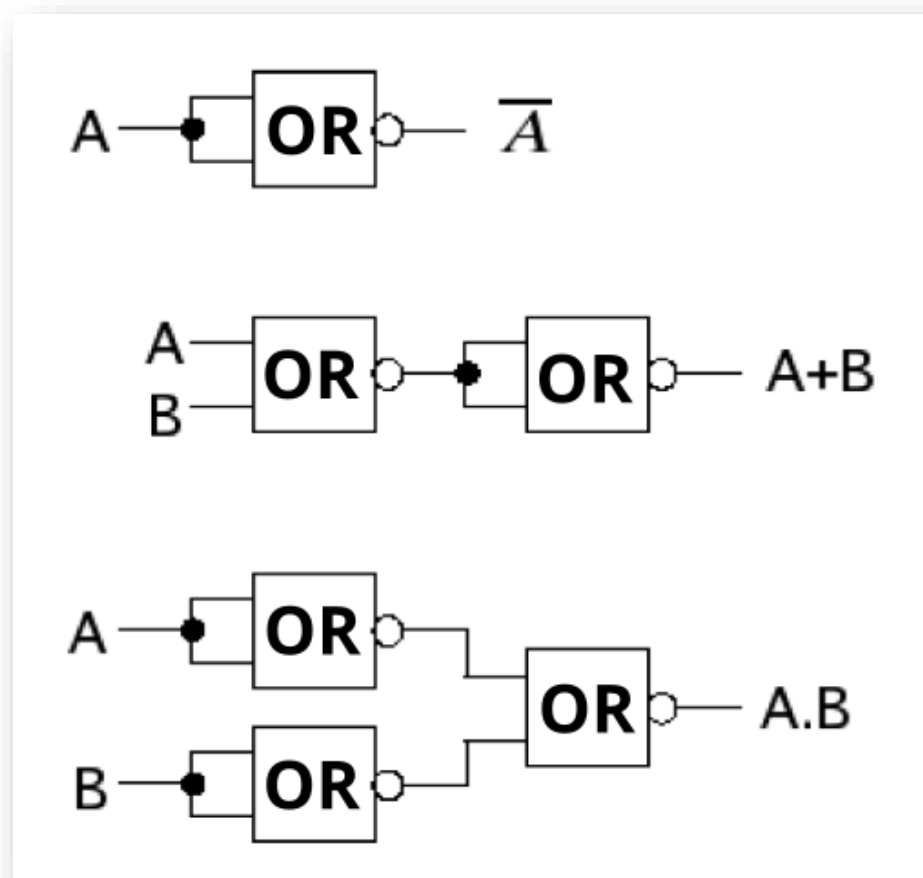- Examples of boolean functions made with NOR gates only:



3) LOGIC CIRCUITS

- Inside the microprocessor, in the control unit and in the Arithmetic and Logic Unit (ALU), electronic circuits are used to create registers, addition, subtraction, multiplication, division, logical operations...
- A logic circuit is an electronic circuit that is dedicated to create a logic function




$$(y_1, \dots, y_m) = f(x_1, \dots, x_n)$$


There is always a delay between the change of the inputs and the update of the outputs

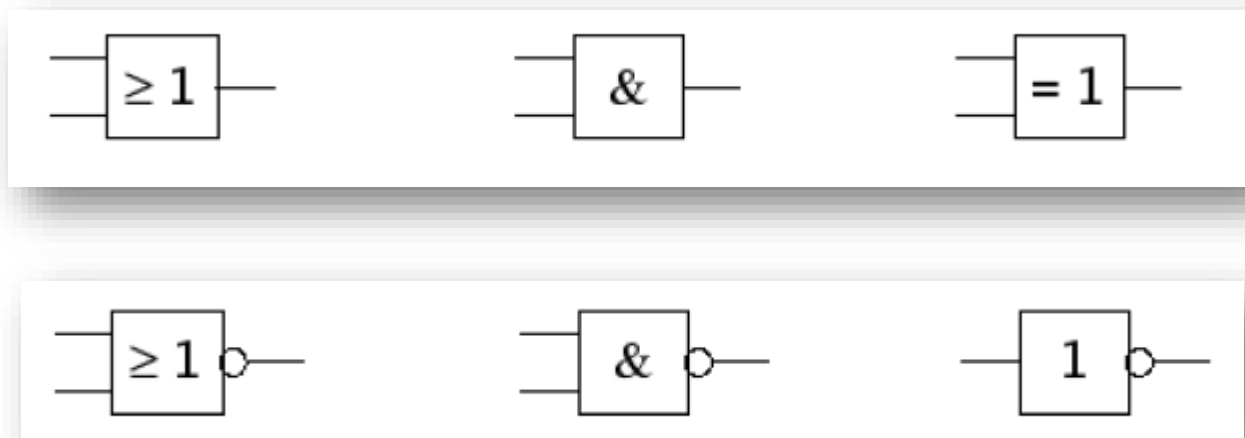3) LOGIC CIRCUITS

- There are two types of logic circuits:
 - **Combinational logic** circuits in which the outputs depend only on the inputs (no internal memorization)
 - **Sequential logic** circuits in which the outputs depend on the inputs and on the previous state of the outputs (internal memorization)




Combinatorial

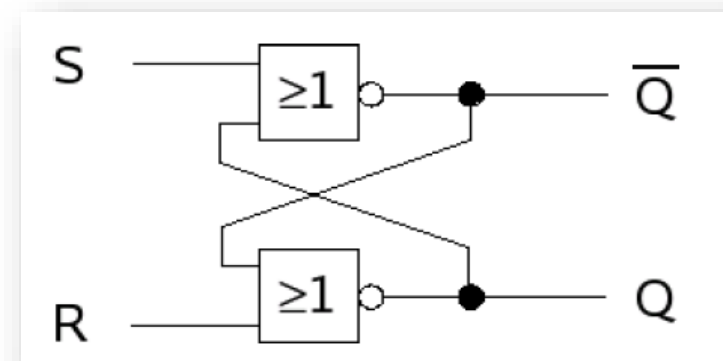

Sequential

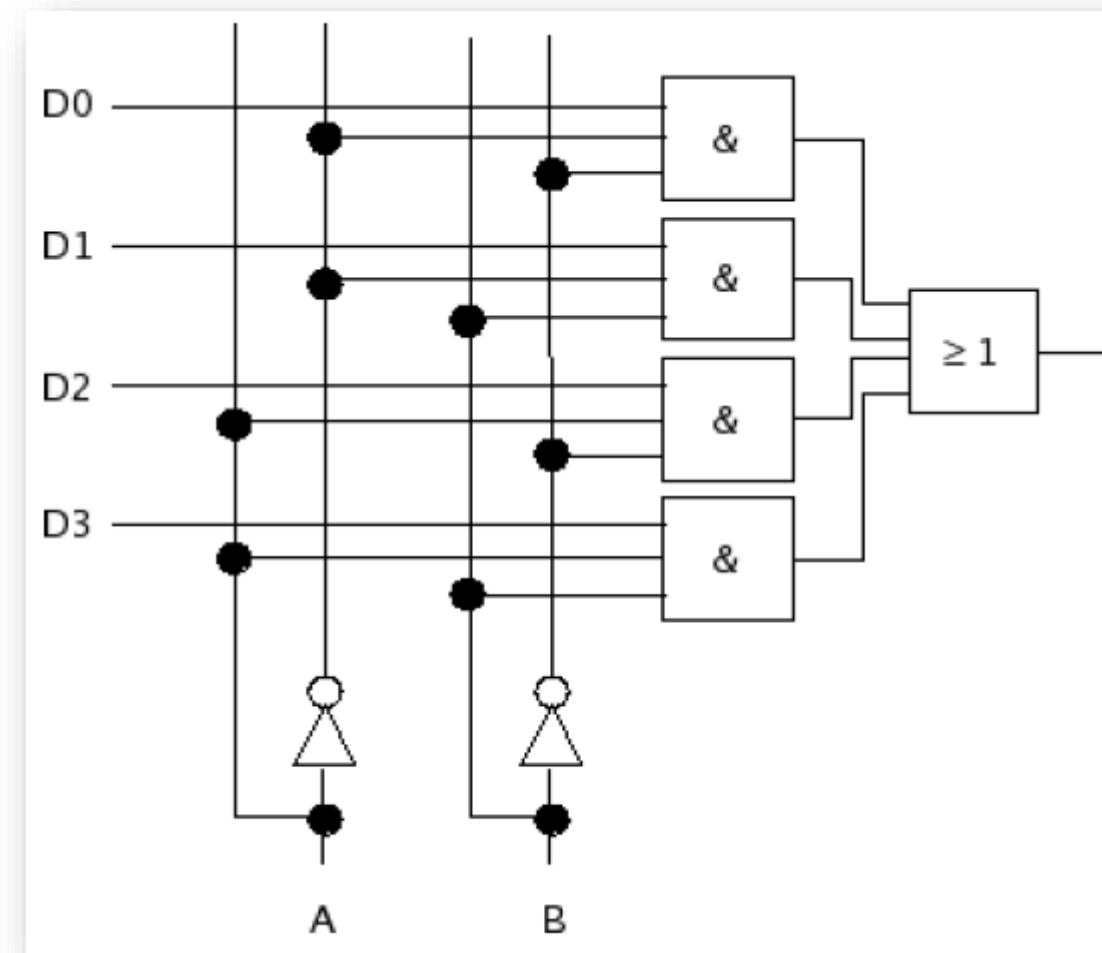3) LOGIC CIRCUITS


- Multiplexer:
 - 2^N inputs
 - 1 output
 - N selection inputs



Combinatorial

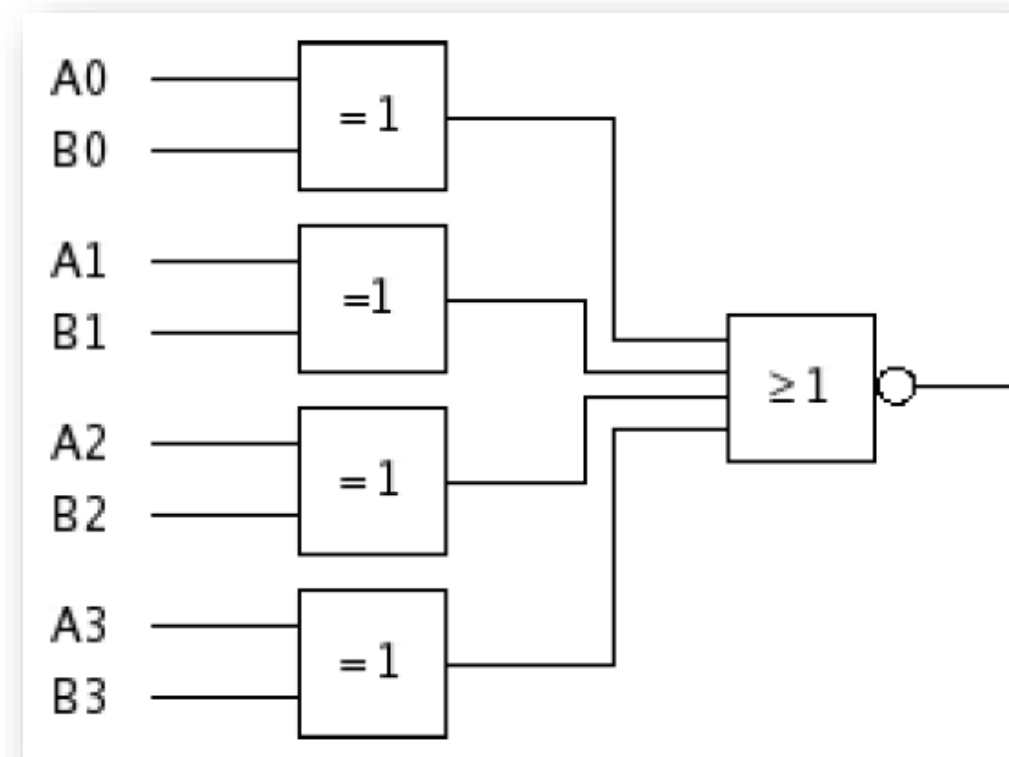3) LOGIC CIRCUITS


- Digital Comparator:
 - $2N$ inputs
 - 1 output
 - Used to compare two binary numbers a , b
 - Output = 1 if $a == b$
 - Output = 0 else



Combinatorial

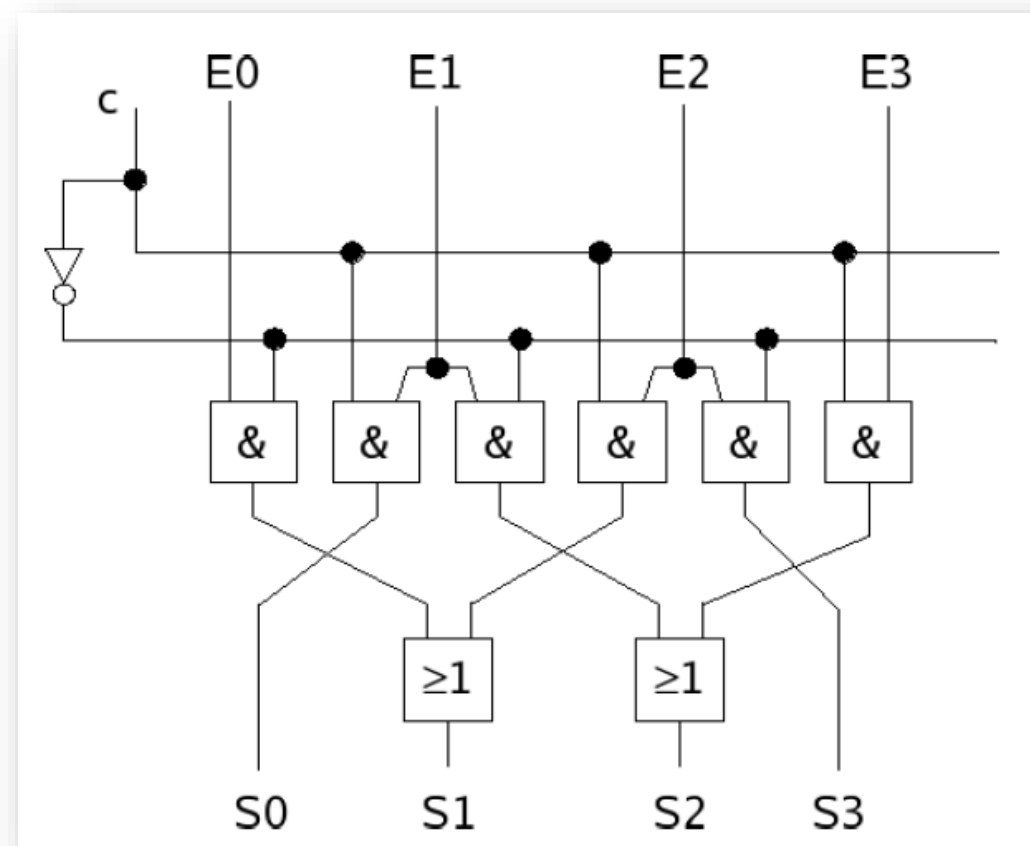3) LOGIC CIRCUITS


- Barrel shifter:
 - 1 command input c
 - 1 input number E (here 4 bits)
 - 1 output number S (here 4 bits)
 - It shifts a binary number to the left or the right depending on the value of c
 - (It is a multiplication or division by 2)




Combinatorial

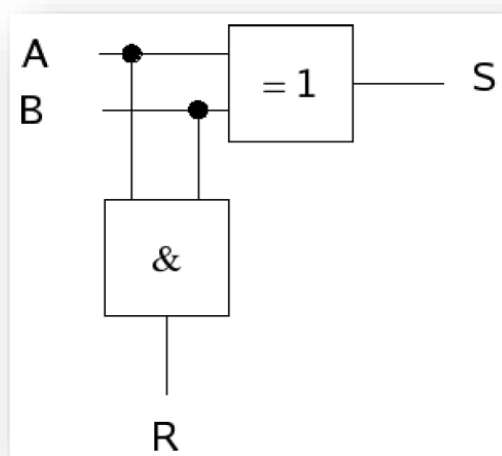3) LOGIC CIRCUITS

- Adder (half-adder and full-adder):
 - Adds two numbers with carry information
 - Adds two numbers with full result



A	B	S	R
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

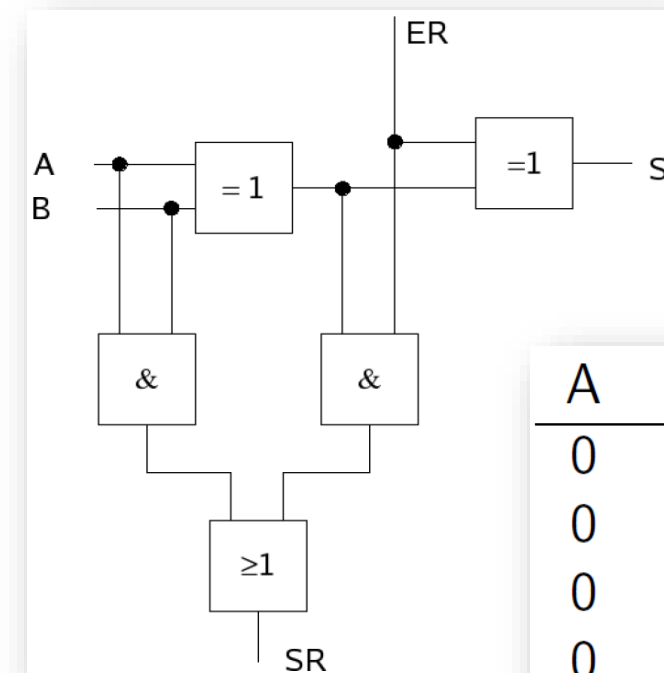


A	B	ER	S	SR
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Combinatorial

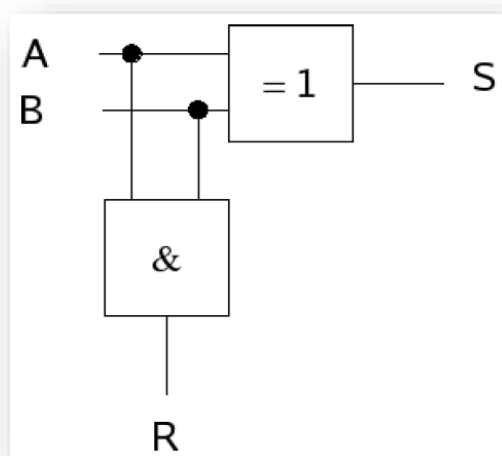3) LOGIC CIRCUITS

- Adder (half-adder and full-adder):
 - Adds two numbers with carry information
 - Adds two numbers with full result



A	B	S	R
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

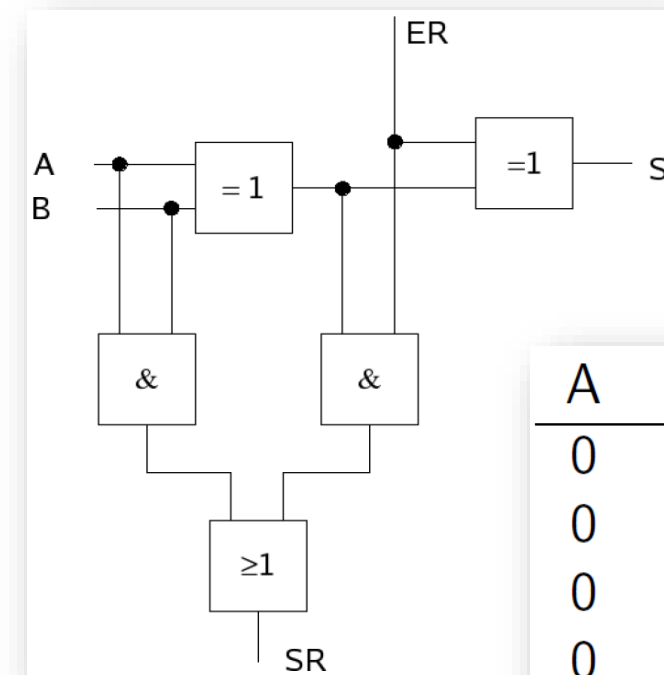

A	B	ER	S	SR
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Combinatorial

3) LOGIC CIRCUITS


- Flip-flops and latches:
 - Sequential circuits to **memorize** one bit state

Sequential

Source: [https://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](https://en.wikipedia.org/wiki/Flip-flop_(electronics))

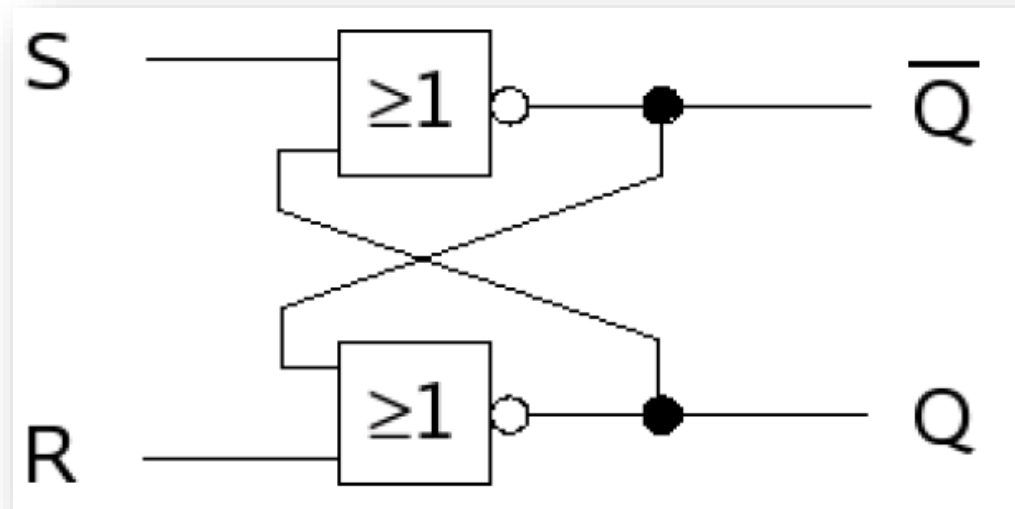3) LOGIC CIRCUITS


- SR NOR latch:
 - Set (S) to put output to 1
 - Reset (R) to put output to 0
 - Problem! When R and S are simultaneously at 1: unstable state => BAD!!!



Sequential

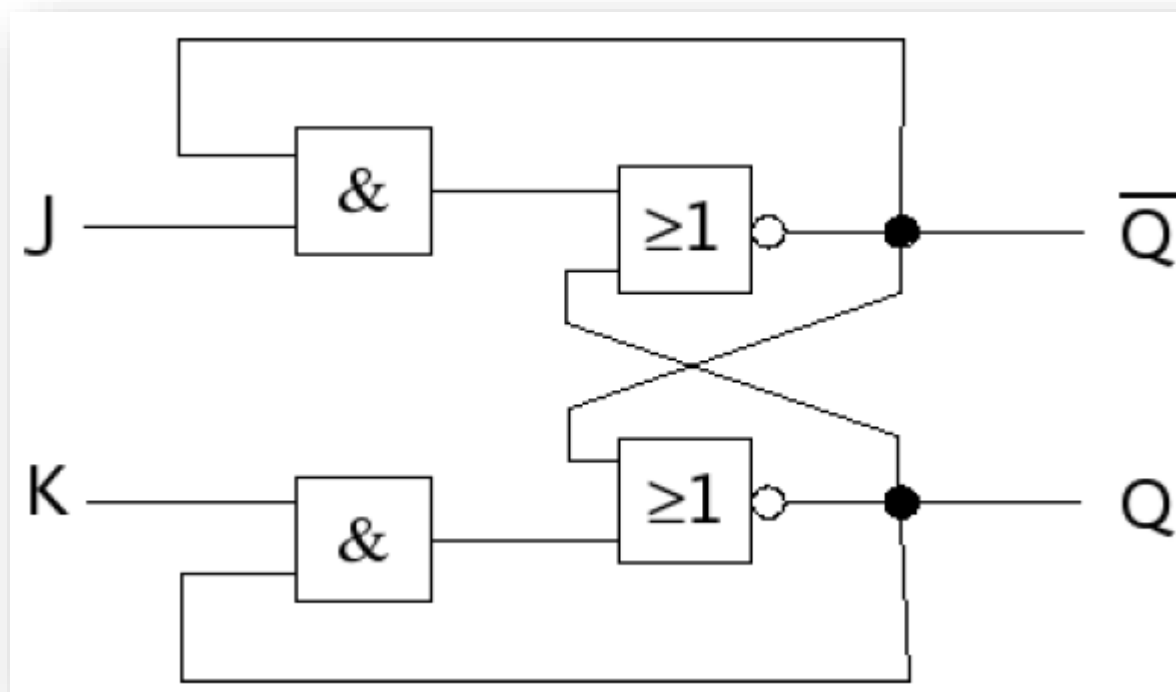3) LOGIC CIRCUITS


- JK latch:
 - No more instability but still two inputs



Sequential

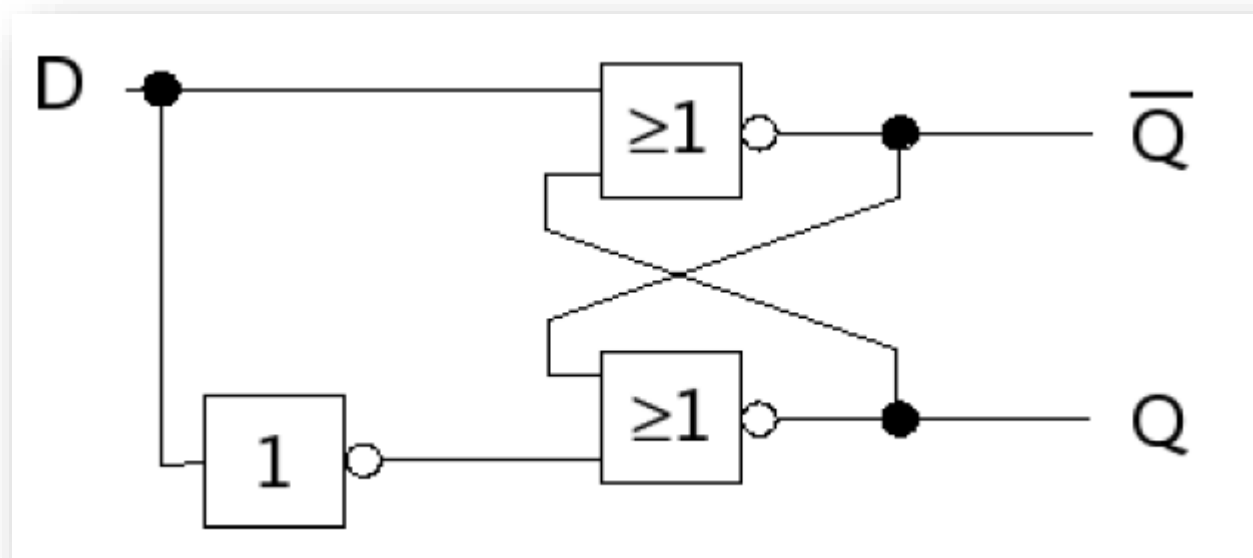3) LOGIC CIRCUITS

- D flip-flop:
 - No more instability and only one input



Sequential

-
- The diagram illustrates the Z80 Architecture, showing the internal components and their interconnections. The architecture is divided into several main sections:
- Control Section:** Contains the Instruction Register, Instruction Decoder, and Control Logic. It also includes a ± 1 block for incrementing or decrementing the PC.
 - Internal Data Bus (8 Bit):** Connects the Control Section to the ALU and the Buffers. It also connects to the MUX and the ± 1 blocks.
 - Address Bus (16 Bit):** Connects the PC to the Buffers. It also connects to the ± 1 blocks.
 - Control Bus:** Connects the Control Section to the Buffers.
 - Registers and ALU:** The ALU (Arithmetic Logic Unit) is connected to the Internal Data Bus and the Address Bus. It includes an ACU (Accumulator) and a TEMP (Temporary) register. The ALU also has a ± 1 block for incrementing or decrementing the PC.
 - Buffers:** There are three buffers: one for the Internal Data Bus, one for the Address Bus, and one for the Control Bus.
- The diagram shows the flow of data and control signals between these components, highlighting the internal structure of the Z80 microprocessor.

ANY QUESTIONS?